

2MBD 26/27

Logic gates problems 1 (Entrega)

$$F_{10} = (A' * B') + (C' * D * A * B') + (C)$$

A	B	C	D	S_{10}
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	0	0	0
11	1	1	1	1
10	1	1	1	1

$$S_1 = \bar{A} \cdot \bar{B}$$

$$S_2 = C$$

$$S_{10} = (\bar{A} \cdot \bar{B}) + C$$

